

```
// 2:1 Multiplexer
```

```
module mux_2_1(
```

```
    input sel,
```

```
    input i0, i1,
```

```
    output y
```

```
);
```

```
    assign y = (sel) ? i1 : i0;
```

```
endmodule
```

```
// Testbench
```

```
module mux_2_1_tb;
```

```
    reg i0, i1, sel;
```

```
    wire y;
```

```
// Instantiate the MUX
```

```
    mux_2_1 uut(
```

```
        .sel(sel),
```

```
        .i0(i0),
```

```
        .i1(i1),
```

```
        .y(y)
```

```
);
```

```
initial begin
```

```
    $monitor("Time=%0t | sel=%b i0=%b i1=%b | y=%b", $time, sel, i0, i1, y);
```

```
// Apply test cases
```

```
    i0 = 0; i1 = 1; sel = 0; #1;
```

```
sel = 1; #1;
```

```
i0 = 1; i1 = 0; sel = 0; #1;
```

```
sel = 1; #1;
```

```
$stop;
```

```
end
```

```
endmodule
```